
 


Multiplexers: 多選一

 


Three-State Buffer: 連接 output



Decoder:

generate all minterms of input variables

 


(priority) Encoder:

從 Y_7 開始看, 如果有 1 就直接 output

ROM: stores an array of binary data

輸入 binary 輸出特定 word

 

Appendix

NOT

AND 乘


OR 加

XOR \oplus 不一樣為 1

XNOR \equiv 一樣為 1

L9

S-R Latch

 


S	R	Q	Q'
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

RQ	0	1
00	0	1
01	1	1
11	0	X
10	0	X

$$Q^* = S + R'Q$$

Gated D Latch

 


G	D	Q	Q'
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

D Flip-Flop: $Q^* = D$ (rising-edge trigger)

D	CK	Q	Q'
D	0→1	X	D
X	0→1	Q	Q


J-K Flip-Flop

 

J	K	Q	Q'
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


$$Q^* = JQ' + K'Q$$

S-R Flip-Flop: $Q^* = S + R'Q$

 

S	R	Operation
0	0	No state change
0	1	Reset Q to 0 (after active CLK edge)
1	0	Set Q to 1 (after active CLK edge)
1	1	Not allowed

T Flip-Flop

 

T	Q	Q'
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^* = TQ' + T'Q$$

Counter Design:

- 畫 Next State table
- 畫 K-map of $C^+ B^+ A^+$

4. 用 Excitation table

結合 Next State table

得出 Flip-Flop equation

$C \rightarrow C^+$ 得 $S_C R_C$

3. 取決於 Flip-Flop 種類: 當 $Q \rightarrow Q^+$ 時 S.R 會是什麼?

Determine the flip flop input equations from the **next-state equations** using K-maps

➤ Always copy X's from next state maps onto input maps first

Type of FF	Input	Q = 0		Q = 1		Rules for forming input map from next state map	
		Q ⁺ = 0	Q ⁺ = 1	Q ⁺ = 0	Q ⁺ = 1	Q = 0 Half of Map	Q = 1 Half of Map
D	D	0	1	0	1	No change	No change
T	T	0	1	1	0	No change	Complement
S-R	S	0	1	0	X	No change	Replace 1's with X's
	R	X	0	1	0	Replace 0's with X's Replace 1's with 0's	Complement
J-K	J	0	1	X	X	No change	Fill in with X's
	K	X	X	1	0	Fill in with X's	Complement

State Table

- Determine the flip-flop input equations and the output equations from the circuit
- Derive the next-state equation for each flip-flop from its input equations
- Plot a next-state map for each flip-flop
- Combine these maps to form the state table


Moore:

output depend on present state

Mealy:

depend on present state & input

AB	A ⁺ B ⁺		Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₀	S ₁	0	1
S ₁	S ₁	S ₂	1	0
S ₂	S ₂	S ₀	0	1
S ₃	S ₃	S ₁	0	1

 

L13

L12

L11

□ Designing a sequential circuit

- Construct a state graph or state table (Unit 14)
- Simplify it (Unit 15)
- Derive flip-flop input equations and output equations (Unit 12)

Construct a state graph (L14)

□ Steps

- Construct sample sequences to help you understand the problem
- Determine under what conditions it should reset
- If only one or two sequences lead to a nonzero output, construct a partial state graph
 - Another way, determine what sequences or groups of sequences must be remembered by the circuit and set up states accordingly
- Each time you add an arrow to the state graph, determine whether it can go to one of the previously defined states or whether a new state must be added
- Check your graph to make sure there is one and only one path leaving each state for each combination of values of the input variables
- When your graph is complete, verify it by applying the input sequences formulated in step 1

Implication Table

□ Draw an empty table, where each square represents a pair

□ If outputs are different, give it an X (impossible!)

□ Write down the implied pair in the square

□ Delete self-implied pairs (redundant)

Present State	Next State		Present Output
	X = 0	X = 1	
A	D	C	0
B	F	H	0
C	E	D	1
D	A	E	0
E	C	A	1
F	F	B	1
G	B	H	0
H	C	G	1

如果 A = B
那麼 D = F, C = H (不可能)


B	D-F C-H						
C	X	X					
D	A-D C-E	A-F E-H	X				
E	X	X	C-E A-D	X			
F	X	X	B-F B-D	X	C-F A-B		
G	B-D C-H	B-F	X	A-B E-H	X	X	
H	X	X	C-E D-G	X	A-G C-F B-G		X
	A	B	C	D	E	F	G

問化 (L15)

Find equivalent state !

"Another" state graph for "0101/1001" sequence detector

➤ Consider all cases

 

Input Sequence	Present State	Next State		Present Output	
		X = 0	X = 1	X = 0	X = 1
Reset	A	B	C	0	0
0	B	D	E	0	0
1	C	F → E	G → D	0	0
00	D	H	I → H	0	0
01	E	J	K → H	0	0
10	F	L → J	M → H	0	0
11	G	N → H	P → H	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0

□ One-hot state assignment: One flip-flop for each state

➤ Example: 3 flip-flops for 3 states ($Q_0Q_1Q_2$)

• $S_0 = 100, S_1 = 010, S_2 = 001$

➤ Write next-state and output (Z) equations directly by inspecting the state graph

• $Q_0^+ = F'R'Q_0 + F'RQ_1 + FQ_2$

• $Q_1^+ = F'R'Q_1 + F'RQ_2 + FQ_0$

• $Q_2^+ = F'R'Q_2 + F'RQ_0 + FQ_1$

• $Z = Z_0Q_0 + Z_1Q_1 + Z_2Q_2$

