

# Midterm

● Graded

Student

PO-YUN) 鄭博允 (CHENG

Total Points

76 / 100 pts

Question 1

Question 1

8 / 8 pts

✓ + 8 pts Correct

+ 6 pts One minor mistake

+ 4 pts Multiple minor mistakes

+ 2 pts Some reasonable effort (incorrect proof)

+ 0 pts Totally wrong or empty

## Question 2

### Question 2

8 / 8 pts

✓ **+ 8 pts** Correct

**+ 7 pts** 1 mistake

**+ 6 pts** 2 mistakes

**+ 5 pts** 3 mistakes

**+ 4 pts** 4 mistakes

**+ 3 pts** 5 mistakes

**+ 2 pts** 6 or more mistakes

**+ 0 pts** Totally wrong or empty

### Question 3

#### Question 3

16 / 16 pts

✓ + 8 pts 3.1. Correct

+ 6 pts 3.1. One minor mistake

+ 4 pts 3.1. Two minor mistakes or one major mistake

+ 2 pts 3.1. Some reasonable effort

+ 0 pts 3.1. Totally wrong or empty

✓ + 8 pts 3.2. Correct

+ 6 pts 3.2. One minor mistake

+ 4 pts 3.2. Two minor mistakes or one major mistake

+ 2 pts 3.2. Some reasonable effort

+ 0 pts 3.2. Totally wrong or empty

## Question 4

### Question 4

8 / 8 pts

✓ **+ 8 pts** Correct (#1,#3,#4,#6,#9) and minimum

**+ 7 pts** Correct (#1,#3,#4,#6,#9) with one incorrect answer

**+ 6 pts** Correct but not minimum

**+ 4 pts** Incorrect with #1 and #3

**+ 2 pts** Some reasonable effort

**+ 0 pts** Totally wrong or empty

## Question 5

## Question 5

Resolved 4 / 8 pts

**+ 8 pts** Correct (0,  $A'B$ ,  $AB'$ ,  $AB$ ,  $A$ ,  $B$ ,  $A'B+AB'$ ,  $A+B$ ).

**+ 6 pts** 1 mistake (e.g., missing 1 correct expression)

**+ 4 pts** 2 mistakes (e.g., missing 2 correct expressions or having 2 incorrect expressions)

✓ **+ 4 pts** 1 major mistake (e.g., listing all 16 expressions, list all 8 expressions without minimization)

**+ 3 pts** 3 mistakes (e.g., missing 3 correct expressions)

**+ 2 pts** At least 1 correct expression

**+ 1 pt** Some reasonable effort

**+ 0 pts** Totally wrong or empty

🔄 Regrade  
Request

Submitted on: Apr 17

教授好，打擾了。

關於第五題，我認為我的算法並沒有錯，答案也是對的，只是沒有經過簡化，然而即便沒有簡化，結果也會是一樣的，例如我的答案

$AB+A'B+AB'$  和正確的答案  $A+B$  實際上兩者是等價的。

因此我認為此題應該視為忘記簡化而斟酌扣分，

而不是視為缺少正確答案或是給出錯誤答案而只有2分。

感謝教授。

We have decided to give 4 points for correct functions without minimization.

Reviewed on: Apr 20

### Question 6

#### Question 6

8 / 8 pts

✓ + 8 pts Correct

+ 6 pts 1 mistake

+ 4 pts 2 mistakes

+ 2 pts 3 mistakes

### Question 7

#### Question 7

8 / 8 pts

✓ + 8 pts Correct

+ 6 pts 1 mistake

+ 4 pts 2 mistakes

+ 2 pts Some reasonable effort

+ 0 pts Totally wrong or empty



## Question 8

### Question 8

6 / 16 pts

+ 8 pts 8.1. Correct

+ 6 pts 8.1. One minor mistake

✓ + 4 pts 8.1. Two minor mistakes or one major mistake

+ 2 pts 8.1. Some reasonable effort

+ 0 pts 8.1. Totally wrong or empty

+ 8 pts 8.2. Correct

+ 6 pts 8.2. One minor mistake

+ 4 pts 8.2. Two minor mistakes or one major mistake

✓ + 2 pts 8.2. Some reasonable effort

+ 0 pts 8.2. Totally wrong or empty

## Question 9

### Question 9

2 / 10 pts

+ 10 pts Correct

+ 8 pts Almost correct (no generalization)

+ 6 pts True with a correct (3-gate) but  
non-generalizable  
counterexample

+ 4 pts True with a wrong  
counterexample

+ 2 pts True (only)

✓ + 2 pts False with some reasonable effort

+ 0 pts Totally wrong or empty

- 2 pts A minor mistake (check comments  
below)

## Question 10

### Question 10

8 / 10 pts

+ 10 pts Correct

✓ + 8 pts Almost correct (show a correct counterexample and the understanding of PI/EPI but consider " $\leq$ " instead of " $<$ ")

+ 6 pts False with some reasonable effort

+ 4 pts True with a good direction

+ 2 pts True with some reasonable effort

+ 2 pts False with a totally wrong counterexample

+ 0 pts Totally wrong or empty

# CSIE 2344, Spring 2023: Midterm

Name: 鄧博允

SID: B11902038

Email: b11902038@csie.ntu.edu.tw


## 1 Boolean Algebra (8pts)

Prove  $A(B \oplus C) = (AB) \oplus (AC)$ , where  $\oplus$  is XOR.

$$\begin{aligned}
 A(B \oplus C) &= A(B'C + BC') &= (AC)(AB)' + (AB)(AC)' \\
 &= AB'C + ABC' &= (AB) \oplus (AC) \\
 &= A'A'C + AB'C + A'AB + ABC' &\text{Q.E.D.} \\
 &= AC(A' + B') + AB(A' + C')
 \end{aligned}$$
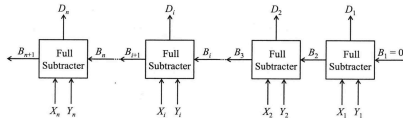
## 2 Full Subtractor (8pts)

A parallel subtractor for  $(X - Y)$  is shown below. A full subtractor has three inputs  $X_i, Y_i, B_i$  and two outputs  $D_i, B_{i+1}$ . Complete the following truth table. No explanation is required.



$X_i$	$Y_i$	$B_i$	$B_{i+1}$	$D_i$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

### 3 Karnaugh Maps (16pts)

Given a Boolean function  $F(A, B, C, D) = \sum m(9, 11, 12, 13) + \sum d(1, 3, 4, 5, 14)$ .

1. (8pts) Find a minimum sum-of-products expression for  $F$ . Only the Karnaugh Map and the final expression are required.

CD \ AB	00	01	11	10
00	0	X	1	0
01	X	X	1	1
11	X	0	0	1
10	0	0	X	0

A:  $F = BC' + B'D$

2. (8pts) Find a minimum product-of-sums expression for  $F$ . Only the Karnaugh Map and the final expression are required.

CD \ AB	00	01	11	10
00	0	X	1	0
01	X	X	1	1
11	X	0	0	1
10	0	0	X	0

$F' = BC + B'D'$

A:  $F = (B' + C')(B + D)$

#### 4 Quine-McCluskey Method (8pts)

Given all prime implicants (PIs) in the following table, list the labels of the selected prime implicants (PIs) for a minimum sum-of-products expression. No explanation is required.

Label	PI	0	4	8	10	12	16	17	21	23	26	30	31
#1	(0,4,8,12)	x	x	x		x							
#2	(0,16)	x					x						
#3	(10,26)				x						x		
#4	(16,17)						x	x					
#5	(17,21)							x	x				
#6	(21,23)								x	x			
#7	(23,31)									x		x	
#8	(26,30)										x	x	
#9	(30,31)											x	x

A: #1 #3 #4 #6 #9

#### 5 Boolean Functions (8pts)

Given a Boolean function  $F(A,B)$ , where  $F(0,0) = 0$ , list the minimum sum-of-products expressions for all possible Boolean functions  $F(A,B)$ . No explanation is required.

A	B	0	1	2	3	4	5	6	7
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	0	1	1	0	1	0	1





  

0	AB	AB'	AB+AB'	AB	A'B+AB	A'B+AB'	AB+A'B+AB'
---	----	-----	--------	----	--------	---------	------------

A: 0 AB+AB'  
 AB AB+A'B  
 AB' A'B+AB'  
 A'B AB+A'B+AB'


## 6 Two-Level Circuit Conversion (8pts)

Draw the following four different two-level gate circuits to realize  $F(A, B, C) = A(B+C)$ . No explanation is required.


1. (2pts) OR-AND	2. (2pts) NOR-NOR
	
3. (2pts) NAND-AND	4. (2pts) AND-NOR
	
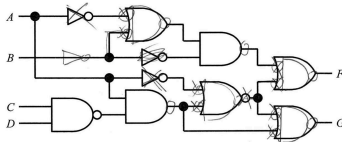
## 7 Multi-Level Circuit Conversion (8pts)

Convert the following circuit *directly* (not from a Karnaugh Map) to a four-level circuit containing only NAND gates (NOT gates are not allowed) and circuit inputs  $A, B, C, D$  ( $A', B', C', D'$  are not allowed as circuit inputs). The number of NAND gates should be 8. No explanation is required.



Draw Your Circuit Below

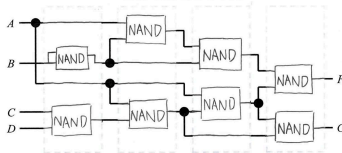


$$F' = BC'D' + BC'D + A'B'D'$$

## 8 Static Hazards (16pts)


Given a Boolean function  $F(A, B, C, D) = (B' + C + D)(B' + C + D')(A + B + D)$ .

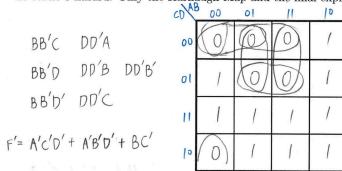1. (8pts) Find a minimum product-of-sums expression for  $F$ , where the corresponding gate circuit has no static-0 hazard. Only the Karnaugh Map and the final expression are required.



$F = (A+C+D)(B'+C+D)(B'+C+D')(A+B'+C)(A'+B'+C)(A+B+D)$

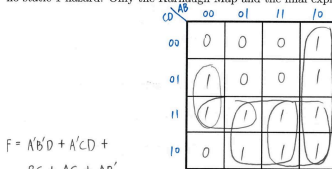2. (8pts) Find a minimum product-of-sums expression for  $F$ , where the corresponding gate circuit has no static-1 hazard. Only the Karnaugh Map and the final expression are required.





## 9 Dynamic Hazards (10pts)

In the examples of dynamic hazards in the lecture and the discussion, there are three changes of the circuit output. Here, we are considering  $2n + 1$  changes of the circuit output.


### Assumptions:

- There is only one circuit input.
- There is only one circuit output.
- There are only four types of gates: {NOT, AND, OR, XOR}.
- A NOT gate has exactly one gate input.
- An AND gate, an OR gate, or an XOR gate has exactly two gate inputs.
- All gates have the same positive propagation delay.

**Statement:** Given the assumptions, it is possible to use only  $2n + 1$  gates to let one change of the circuit input results in  $2n + 1$  changes of the circuit output.

Answer if the statement is True or False and then draw a corresponding gate circuit (if True) or prove it (if False).

False.

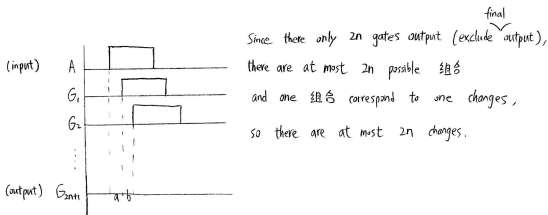

## 10 Prime Implicants and Essential Prime Implicants (10pts)

The *size* of an implicant is defined as the number of minterms covered by the implicant. For example, given a Boolean function  $F(A, B, C, D) = ABCD + A'B'C'$ , the size of  $ABCD$  is 1, and the size of  $A'B'C'$  is 2.

Also, the *total-size* of a function is defined as the summation of the sizes of all prime implicants of the function. For example, given a Boolean function  $F(A, B, C, D) = ABCD + A'B'C'$ , the total-size of  $F$  is 3.

**Statement:** given a Boolean function  $F(A, B, C, D)$ , if all of its prime implicants are essential prime implicants, then the total-size of  $F$  is smaller than 32.

Answer if the statement is True or False and then prove it (if True) or find a counterexample (if False).

True.

The max size of an implicant is 8, such implicant are  $A, A', B, B', C, C', D, D'$

Since  $A+A'=1$  can be ignore,

the max total-size of  $F(A, B, C, D)$  happened when  $F = (A/A') + (B/B') + (C/C') + (D/D')$

and it's 32.

so the statement is true.

