

# Final Exam

● Graded

Student

PO-YUN) 鄭博允 (CHENG

Total Points

62 / 100 pts

## Question 1

### Question 1

24 / 28 pts

✓ **+ 28 pts** Correct

– 2 pts A mistake in Q1.1

– 2 pts A mistake in Q1.2

– 2 pts A mistake in Q1.3

– 2 pts A mistake in Q1.4

– 2 pts A mistake in Q1.5

– 2 pts A mistake in Q1.6

– 2 pts A mistake in Q1.7

✓ **– 4 pts** Multiple mistakes in Q1.1

– 4 pts Wrong in Q1.6

– 4 pts Wrong in Q1.7

## Question 2

### Question 2

0 / 6 pts

+ 6 pts Correct

+ 4 pts Correct when  $L = 1$  and  $H = 1$   
(Cycles 1, 2, 3, 5)

+ 4 pts Correct when  $L = 1$  and  $(L, H) = (0, 0)$  (Cycles 1, 4, 5)

+ 2 pts Correct when  $L = 1$  (Cycles 1, 5)

+ 2 pts Correct when  $H = 1$  (Cycles 2, 3)

+ 2 pts Correct when  $(L, H) = (0, 0)$  (Cycle 4)

✓ + 0 pts Totally wrong or empty

### Question 3

### Question 3

8 / 8 pts

✓ **+ 8 pts** Correct ( $C, 0, C'+DE, C'D'+CE$ )

**+ 6 pts** 1 minor mistake (not minimum or wrong for  $(A, B) = (1, 1)$ )

**+ 6 pts** 1 minor mistake (floating or wrong for  $(A, B) = (0, 1)$ )

**+ 4 pts** 2 minor mistakes or 1 major mistake

**+ 2 pts** Reasonable effort

**+ 0 pts** Totally wrong or empty

## Question 4

### Question 4

12 / 12 pts

✓ **+ 8 pts** 4.1. Correct

**+ 6 pts** 4.1. One mistake (one of A+, B+, or Z)

**+ 4 pts** 4.1. Two mistakes (two of A+, B+, or Z)

**+ 2 pts** 4.1. Reasonable effort

✓ **+ 4 pts** 4.2. Correct

**+ 2 pts** 4.2. One mistake or no output

**+ 0 pts** Totally wrong or empty

## Question 5

### Question 5

8 / 8 pts

+ 8 pts Correct

✓ + 8 pts Correct (with equivalent states)

+ 6 pts 1 minor mistake

+ 4 pts 1 major mistake or 2 minor mistakes

+ 2 pts Reasonable effort

+ 0 pts Totally wrong or empty

## Question 6

### Question 6

0 / 8 pts

- + 8 pts Two solutions
- + 6 pts Two solutions and one without sufficient explanation
- + 4 pts Two solutions and both without sufficient explanation
- + 4 pts Two equivalent or similar solutions
- + 4 pts One solution
- + 2 pts Some reasonable effort (e.g., increase the propagation delay of the combinational circuit)

✓ + 0 pts Totally wrong or empty

## Question 7

### Questions 7.1-7.3

4 / 6 pts

+ 6 pts Correct

✓ + 4 pts One mistake

+ 2 pts Two mistakes

+ 0 pts Totally wrong or empty

## Question 8

### Question 7.4

0 / 6 pts

+ 6 pts True with correct explanation

+ 4 pts True with almost-correct explanation

+ 2 pts True only

+ 2 pts False with reasonable effort

✓ + 0 pts False only or empty



## Question 9

## Question 8

2 / 8 pts

+ 8 pts Yes with correct explanation

+ 6 pts Yes with almost-correct explanation

+ 6 pts Yes with almost-correct explanation (gate/propagation delay)

+ 4 pts Yes with reasonable explanation

+ 4 pts Yes with reasonable explanation (useless if changing during the first half)

+ 4 pts Yes with reasonable explanation (similar to S-R FF)

+ 2 pts Yes only

✓ + 2 pts No with reasonable explanation

+ 0 pts No only or empty

## Question 10

## Question 9

4 / 10 pts

+ 10 pts "T flip-flops last" with correct explanation

+ 8 pts "T flip-flops last" with almost-correct explanation

+ 6 pts "T flip-flops last" with reasonable effort

+ 4 pts "T flip-flops last" without explanation

+ 6 pts "T flip-flops middle" with good explanation

✓ + 4 pts "T flip-flops middle" with reasonable effort

+ 2 pts "T flip-flops middle" with wrong explanation

+ 2 pts "T flip-flops first" with reasonable effort

+ 0 pts "T flip-flops first" without explanation

+ 0 pts Empty

# CSIE 2344, Spring 2023: Final Exam

Name: 鄭博允

SID: B11902038

Email: b11902038@csie.nthu.edu.tw

## 1 Counter Design (28pts)

Design a 3-bit counter which counts  $CBA$  in the sequence: 001, 010, 110, 111, 100, 011, and repeats. If the counter is initialized as 101, it should count to 001 and then follow the sequence.

- (4pts) Complete the following truth table.
- (4pts) Complete the following Karnaugh map for  $B^+$ .
- (4pts) Complete the following Karnaugh map for  $A^+$ .
- (4pts) Use an S-R flip-flop and complete the following Karnaugh map for  $R_B$ .
- (4pts) Use a J-K flip-flop and complete the following Karnaugh map for  $K_A$ .
- (4pts) Derive a minimum sum-of-products expression for  $R_B$ .  $R_B = BC$
- (4pts) Derive a minimum sum-of-products expression for  $K_A$ .  $K_A = B'C'$


No explanation is needed.

C	B	A	C'	B'	A'
0	0	0	X	X	X
0	0	1	0	1	0
0	1	0	1	1	0
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	X	X	X

C	B	A	C'	B'	A'
0	0	1	0	1	0
0	1	1	0	1	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	0	0	1
1	1	1	0	0	1
1	1	1	0	0	1
 
## 2 Parallel-In Parallel-Out (PIPO) Right Shift Register (6pts)

Given the following PIPO right shift register, complete the following table. No explanation is needed.




Clock Cycle	L	H	SI	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub> =SO
1	1	0	0	1	0	0	0	/	0	0	0
2	0	1	1	0	1	0	1	0	/	0	0
3	0	1	0	1	0	1	0	/	0	/	0
4	0	0	1	1	1	1	1	0	/	0	/
5	1	0	0	0	0	0	0	/	0	/	0
 
## 3 Multiplexer (8pts)

Draw a circuit for  $F(A, B, C, D, E) = A'B'C + AB'C' + AB'DE + ABC'D' + ABD'E + ABCE$  with the following requirements. No explanation is needed.

- There is exactly one multiplexer, and the multiplexer has 2 control inputs and 4 data inputs.
- The control inputs are  $A$  and  $B$ .
- Each data input is a minimum sum-of-products (AND-OR) circuit of  $C$ ,  $D$ , and  $E$ .




#### 4 Circuit Analysis (12pts)


Given the circuit including one D flop-flop and one T flop-flop.

- (8pts) Complete the following transition table.
- (4pts) Draw the corresponding state graph where a state  $S_{ij}$  represents the state  $(A, B) = (i, j)$ .

No explanation is needed.

 


AB	$A^+B^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
00	01	11	0	1
01	01	01	1	1
11	00	00	1	1
10	01	11	0	0

 
 
## 5 State Graph Derivation (8pts)


Draw the state graph of a Mealy machine with one input and one output. If the input is 0 following a sequence of "exactly" one 0 input (not two or more 0's) and one 1 input (not two or more 1's), the output is 1; otherwise, the output is 0. Example:


 
## 6 Setup Time (8pts)

Setup time is the amount of time that a flip-flop must be stable before the active edge. Considering the following sequential circuit, if the setup time of the second flip-flop (FF2) is violated, how to fix it without changing the flip-flops?

- (4pts) List two solutions.
- (4pts) Explain the reasons.





## 7 State Equivalence and Circuit Equivalence (12pts)

Answer if the statements are True or False by circling the correct choices. No explanation is needed.

- ☒ T F 1. (2pts) For a 1-bit input  $X$ , if the outputs of two states are not equal, then the two states are not equivalent.
- T ☒ F 2. (2pts) For a 1-bit input  $X$ , if the next states of two states are not equal ("equal" means "the same"), then the two states are not equivalent.
- ☒ T F 3. (2pts) Two equivalent sequential circuits always have the same number of states.

Answer if the statement is True or False and explain the reason.

4. (6pts) Two states  $p$  and  $q$  are equivalent if and only if for each 2-bit input  $X$  and  $Y$ ,


$$\lambda(p, X) = \lambda(q, X) \text{ and } \lambda(\delta(p, X), Y) = \lambda(\delta(q, X), Y) \text{ and } \delta(\delta(p, X), Y) \equiv \delta(\delta(q, X), Y),$$

where  $\lambda()$  is the output and  $\delta()$  is the next state.

## 8 J-K Flip-Flop (8pts)

In the slides of Unit 11, it is mentioned that we should only allow the S and R inputs of a S-R flip-flop to change during the first half of a clock cycle.

 1. (2pts) Given the following implementation of a J-K flip-flop, do we have the same constraint?
2. (6pts) Explain the reason.



1. No

2. This implementation forced two S-R flip-flop working at different period of clock cycle. That is, in the first half of a clock cycle, only the Master S-R flip-flop work, and the Slave S-R flip-flop stay unchanged because both its inputs are 0. In the second half of a clock cycle, the situation reverse.

Therefore, we don't have to restrict the period of change inputs since it doesn't affect the circuit.

## 9 State Assignment (10pts)

In the slides of Unit 15, it is mentioned that the guidelines for state assignment (for example: placing 1's together on an input map) only works for specific flip-flops.

1. (4pts) Sort D, T, and J-K flip-flops by their fitness for the guidelines (for example: answering "D > T > J-K" means that D flip-flops best fit the guidelines, better than T flip-flops, and J-K flip-flops least fit the guidelines).
2. (6pts) Explain the reason. Note that we are not expecting an answer which discusses a specific example.

1. J-K > T > D

2. J-K flip-flop is best fit the guidelines since it has more input-output situations, that is, we can identify different state more easily.

For T flip-flop and D flip-flop, the possible situations are less than J-K flip-flop. Moreover, T > D.

