

NOT \neg AND \wedge 乘OR \vee 加XOR \oplus \rightarrow 不一樣為 1XNOR \oplus \equiv \rightarrow 一樣為 1**LAWS**

duality: AND/OR 互換 · 1/0 互換

Distributive: $X + YZ = (X + Y)(X + Z)$

DeMorgan's: $(X + Y)' = X'Y'$

$(XY)' = X' + Y'$

Another: $(X + Y)(X' + Z) = XZ + X'Y$

$X \oplus Y = X'Y + XY'$

$X \equiv Y = X'Y' + XY$

Uniting: $XY + XY' = X$

$(X + Y)(X + Y') = X$

Absorption: $X + XY = X$

$X(X + Y) = X$

Elimination: $X + X'Y = X + Y$

$X(X' + Y) = XY$

Consensus: $XY + X'Z + YZ = XY + X'Z$

$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

MIN / MAXTERM


SOP: counting 1's

POS: counting 0's (find SOP of F' and DeMorgan's to F)(m) minterm: 每個 variable 都出現一次的 SOP e.g. $m_0 = A'B'C'$ $\overline{X}X' = 0$ (M) maxterm: 同上, 但 POS e.g. $M_0 = A + B + C$

$F = \sum m(3, 4, 5, 6, 7) = \prod M(0, 1, 2) / F' = \sum m(0, 1, 2) = \prod M(3, 4, 5, 6, 7)$


KMAP

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|-------|-------|----------|----------|
| 00 | m_0 | m_4 | m_{12} | m_8 |
| 01 | m_1 | m_5 | m_{13} | m_9 |
| 11 | m_3 | m_7 | m_{15} | m_{11} |
| 10 | m_2 | m_6 | m_{14} | m_{10} |

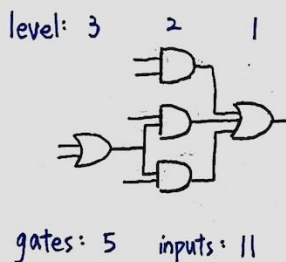
CIRCUITSSOP \rightarrow AND-ORPOS \rightarrow OR-AND

bubbles 往後推

交換 AND-OR

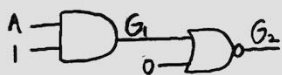NAND \equiv AND-NOT \neg \neg NOR \equiv OR-NOT \neg \neg **TIMING**

propagation delay: 20ms

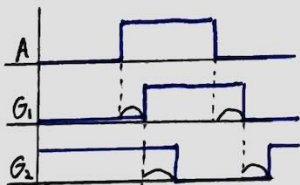**HAZARD**

Static 1-/0-Hazard

output momentarily goes to 0/1 when it should remain a constant 1/0

Dynamic Hazard

output change 3+ times when changes from 0 \rightarrow 1 (1 \rightarrow 0)

Remove static 1-/0-

add additional loops for adjacent 1's / 0's

Avoid: 不能省略 $XX'X$, $X + X' + \beta$ · treat XX' as different variable

分析: static 1-hazard: 看相鄰的 1 有沒有被 loop

static 0-hazard: 看 $XX'X$, adjacent 0's differ in value of X when $X = 1$ dynamic hazard: 看 $XX'X$, adjacent 0 and 1 differ in value of X when $X = 1$ 再看該變化經過的路徑 ≥ 3